



DIGITAL SYSTEM DESIGN APPLICATION PROJECT 6

STATE REDUCTION

a) We prepare table including state,next state input and output. If there are states that the same as next state and output, we can reduction these.and we can delete one of the similar and write not deleted state name to deleted states.

b)

State	next state, output	
	x = 0	x = 1
A	B,0	D,0
B	C,0	D,0
C	C,1	D,0
D	A,0	E,0
E	A,0	F,0
F	A,0	F,1

In this table we can not do reduction. There are not state that have same output and same next state.

STATE ENCODING

There are several methods of encoding state. We decide to which one. gains are effective like Speed, area power consumption. For example type of encoding binary encoding, one – hot encoding, gray encoding . A wrong decision may result in a state machine that uses too much logic, too slow, or both.

State	State Variables		
	One-Hot Code	Binary Code	Gray Code
S0	00001	000	000
S1	00010	001	001
S2	00100	010	011
S3	01000	011	010
S4	10000	100	110

Table 1:An example of state Encoding for a 4 state Machine

b) binary encoding

STATE	NS,X=0	NS, X=1	OUT , X=0	OUT, X=1	BİNARY
A	B	D	0	0	000
B	C	D	0	0	001
C	C	D	1	0	010
D	A	E	0	0	011
E	A	F	0	0	100
F	A	F	0	1	101

Binary encoding. Less flip flop than one-hot. This cause using more power. We give sequential binary code to sequential state name. And changing to table like bottom. $Q = \log_2(n)$, $n=6$ coset number $q=3$

Gates: gray > binary > one-hot

Flipflop: one -hot > binary = gray

Power consumption gray < binary > one-hot

x	q2	q1	q0	Q2	Q1	Q0	z
0	0	0	0	0	0	1	0
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	0	0	0
0	1	0	0	0	0	0	0
0	1	0	1	0	0	0	0
0	1	1	0	k	k	k	k
0	1	1	1	k	k	k	k
1	0	0	0	0	1	1	0
1	0	0	1	0	1	1	0
1	0	1	0	0	1	1	0
1	0	1	1	1	0	0	0
1	1	0	0	1	0	1	0
1	1	0	1	1	0	1	1
1	1	1	0	k	k	k	k
1	1	1	1	k	k	k	k

REDUCTION OF COMBINATORIAL PART

Q_0	000		001		011		010		110		111		101		100	
0	1	0	0	0	0	0	K	K	0	0						
1	1	1	0	1	K	K	1	1								

Q_1	000		001		011		010		110		111		101		100	
0	0	1	0	1	K	K	0	0								
1	1	1	0	1	K	K	0	0								

Q_2	000		001		011		010		110		111		101		100	
0	0	0	0	0	0	0	K	K	0	0						
1	0	0	1	0	K	K	1	1								

Q_3	000		001		011		010		110		111		101		100	
0	0	0	0	1	K	K	0	0								
1	0	0	0	0	K	K	1	0								

Q_4	000		001		011		010		110		111		101		100	
0	0	0	0	1	K	K	0	0								
1	0	0	0	0	K	K	1	0								

Q_5	000		001		011		010		110		111		101		100	
0	0	0	0	1	K	K	0	0								
1	0	0	0	0	K	K	1	0								

Q_6	000		001		011		010		110		111		101		100	
0	0	0	0	1	K	K	0	0								
1	0	0	0	0	K	K	1	0								

Q_7	000		001		011		010		110		111		101		100	
0	0	0	0	1	K	K	0	0								
1	0	0	0	0	K	K	1	0								

Q_8	000		001		011		010		110		111		101		100	
0	0	0	0	1	K	K	0	0								
1	0	0	0	0	K	K	1	0								

Q_9	000		001		011		010		110		111		101		100	
0	0	0	0	1	K	K	0	0								
1	0	0	0	0	K	K	1	0								

Q_{10}	000		001		011		010		110		111		101		100	
0	0	0	0	1	K	K	0	0								
1	0	0	0	0	K	K	1	0								

Q_{11}	000		001		011		010		110		111		101		100	

$$\begin{aligned}
 Q_0 &= x \cdot q_1' + x \cdot q_0' + q_2' q_1' q_0' \\
 Q_1 &= q_1 q_0' + q_2' q_1' q_0 + x q_2' q_1' \\
 Q_2 &= x q_2 + x q_1 q_0 \\
 Q &= x q_1 q_0' + x q_2 q_0
 \end{aligned}$$

B) lut 4)

For Less lut use One – hot encoding .

VERILOG ENCODING

```
`timescale 1ns / 1ps
module FSM1(
    input x,clk,
    output z
);
    reg q0=1'b0,q1=1'b0,q2=1'b0;
    wire Q0,Q1,Q2;
    always@(posedge clk)
    begin
        q0 <= Q0;
        q1 <= Q1;
        q2 <= Q2;
    end

    assign Q0=(~(q2) & ~(q1) & ~(q0)) | (x & ~(q1)) | (x & ~(q0));
    assign Q1=(~(q2) & ~(q1) & x) | (q1 & ~q0) | (~(q2) & ~(q1) & (q0));
    assign Q2=(x & q2) | (x & q1 & q0);
    assign z=(x & q2 & q0) | ((~x) & (~q0) & q1 );
```

testbench

```


`timescale 1ns / 1ps
module experiment6tb;

    reg clk;
    wire z;
    reg x;
    reg [31:0]values;
    reg [9:0]values2;


    FSM1 uut(.x(x),.clk(clk),.z(z));
    integer i;
    initial
    begin
        clk=1'b0;
        values = 32'b010011000111000011110000011111100;
        values2 = 10'b0000111111;
        i=31;
        while(i>=0)
        begin
            clk = ~clk;
            x=values[i];
            #5
            clk <=~clk;
            #5
            i = i-1;
        end
        clk = ~clk;
        x=values2[9]; #5
        clk <=~clk; #5
        clk = ~clk;
        x=values2[8];
        #5 clk <=~clk;
        #5  clk = ~clk; x=values2[7];
        #5clk <=~clk;
        #5  clk = ~clk;x=values2[6];
        #5clk <=~clk;
        #5  clk = ~clk;
        x=values2[5];#5clk <=~clk;
        #5  clk = ~clk;x=values2[4];
        #5clk <=~clk;#5
        clk = ~clk;x=values2[3];
        #5clk <=~clk;
    end
endmodule

```


rtl

 


Technology schematic

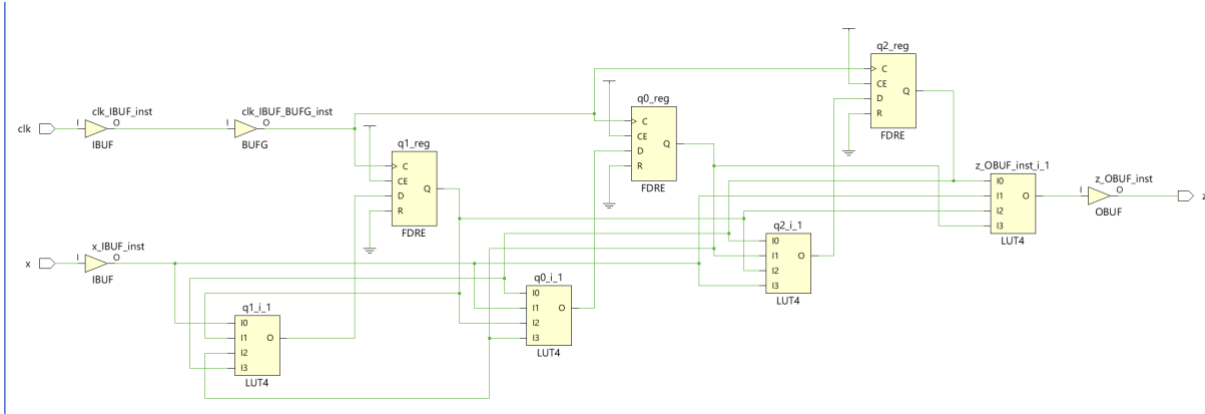


SIMULATION OF THE CIRCUIT

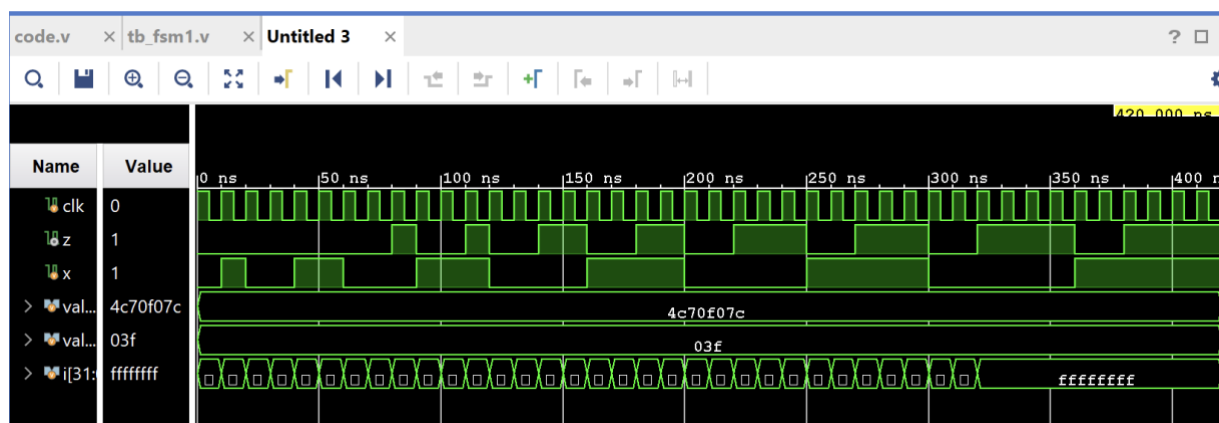


ANALYSIS OF FAULTY OUTPUTS

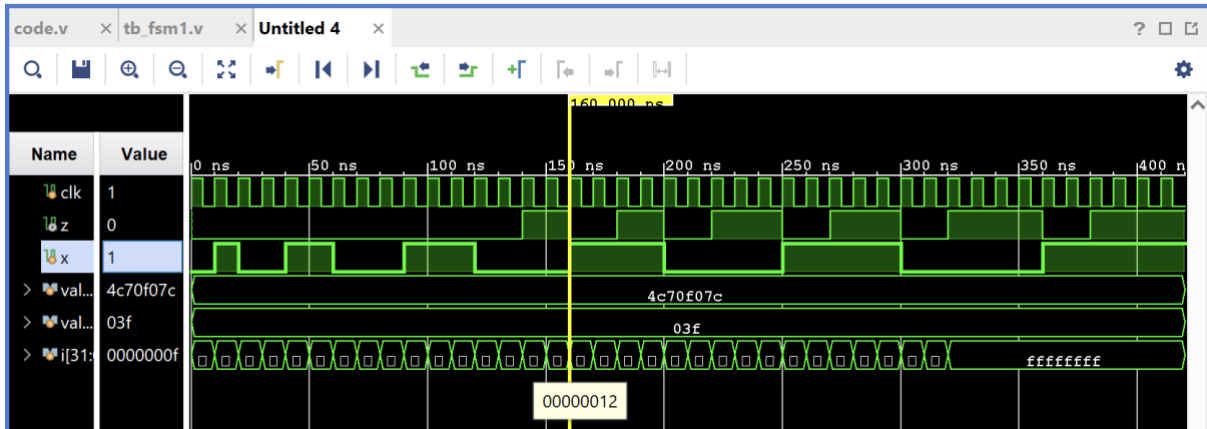


MACHINE TYPE CHANGING

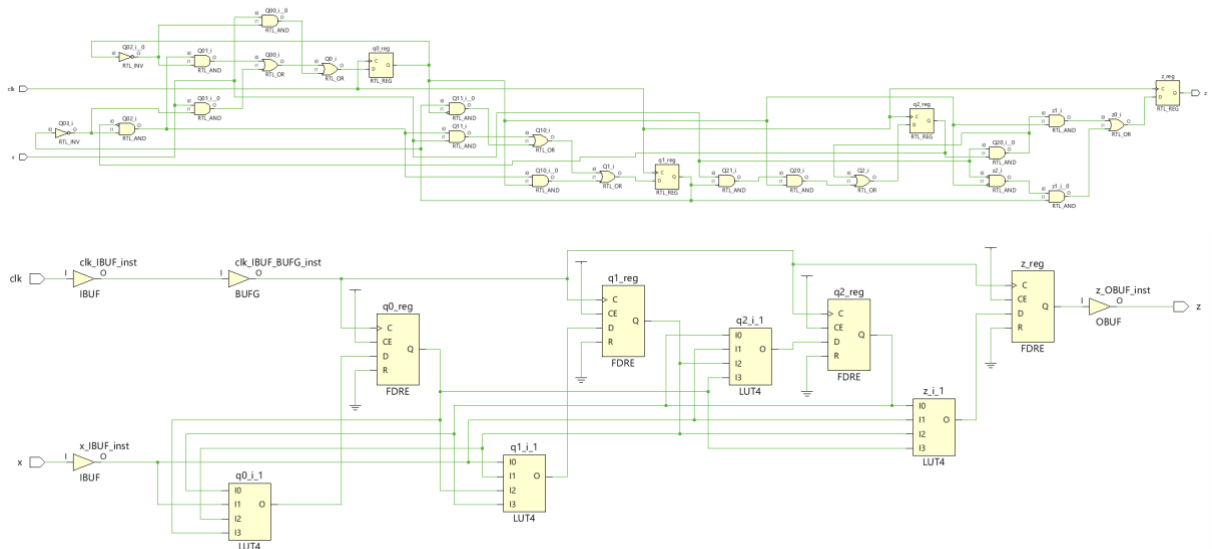

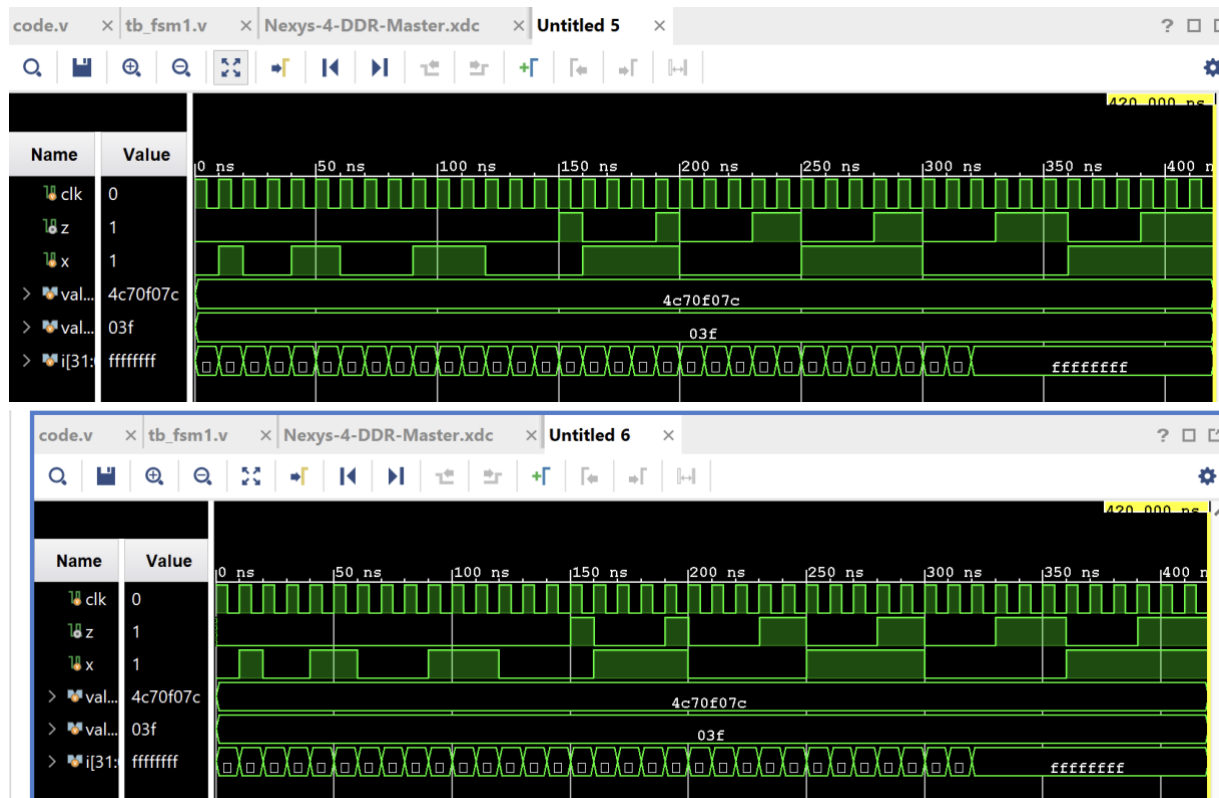

STUCKING IN UNDESIRABLE STATES

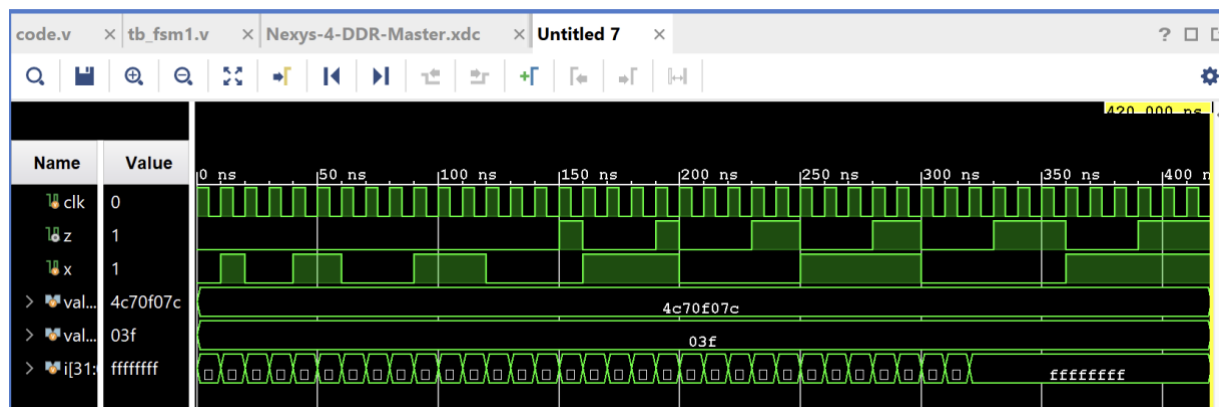

Yes, it is working after undifined state

DESIGN WITH DIVIDED STATE DIAGRAMS