



# DIGITAL SYSTEM DESIGN APPLICATION PROJECT 4

## HALF ADDER

### Half Adder Verilog code


```
module HA(cout,s,x,y);
    input x,y;
    output cout,s;
    xor xor1(s, x,y);
    and and2(cout, x,y);
endmodule
```

### Test code for Half Adder


```
`timescale 1ns / 1ns

module tb_arithmetic_circuit ;
    wire sum, carry;
    reg a, b;
    HA uut(.x(a), .y(b), .s(sum), .cout(carry));
    initial
    begin
        a = 1'b0; b = 1'b0;
        #5
        a = 1'b0; b = 1'b1;
        #5 //3
        a = 1'b1; b = 1'b0;
    end
endmodule
```

### Rtl schema

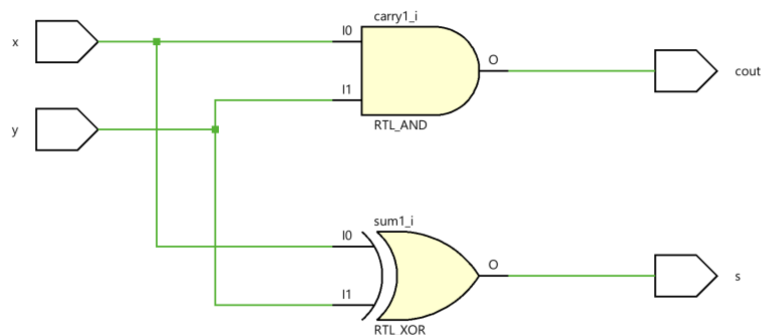

## Technology schema

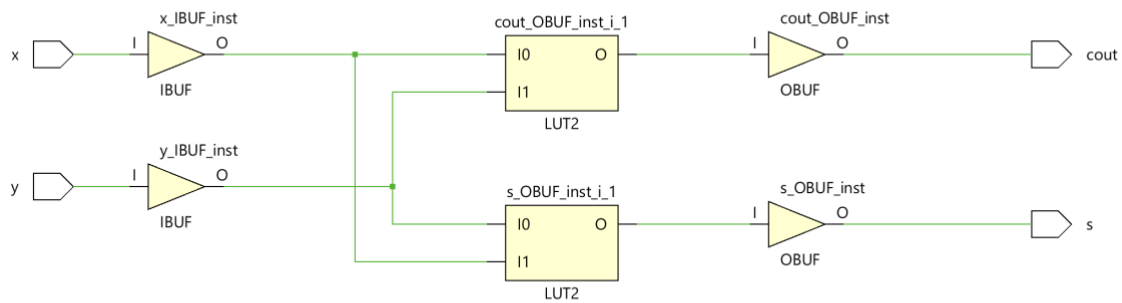

How many luts. = 1

## Delay of circuit

From Port	To Port	Max Delay	Max Process Corner	Min Delay	Min Process Corner
x	cout	5.461	SLOW	2.063	FAST
x	s	5.243	SLOW	1.996	FAST
y	cout	5.690	SLOW	2.131	FAST
y	s	5.461	SLOW	2.065	FAST

## Comments:

We did half adder. Half adder add 1-bit two different input and if there are carry it shows that in cout output

## FULL ADDER


### Full adder verilog code

```
module FA(cout_fa,s_fa,x,y,ci);
    input x,y,ci;
    output cout_fa,s_fa;
    wire sum_1,carry_1,carry_2;
    HA HA1(carry_1,sum_1,x,y);
    HA HA2(carry_2,s_fa,sum_1,ci);
    or or1(cout_fa,carry_2,carry_1);
```


### Test code

```
module tb_fa( );
    wire sum, carry_out;
    reg a, b, c;
    FA uut(.x(a), .y(b), .ci(c), .s_fa(sum), .cout_fa(carry_out));
    initial
    begin
        a = 1'b0; b = 1'b0; c = 1'b0;
        #10; a = 1'b0; b = 1'b0; c = 1'b1;
        #10; a = 1'b0; b = 1'b1; c = 1'b0;
        #10; a = 1'b0; b = 1'b1; c = 1'b1;
        #10; a = 1'b1; b = 1'b0; c = 1'b0;
        #10; a = 1'b1; b = 1'b0; c = 1'b1;
    end
```

### Rtl schema

 

## Technology schema

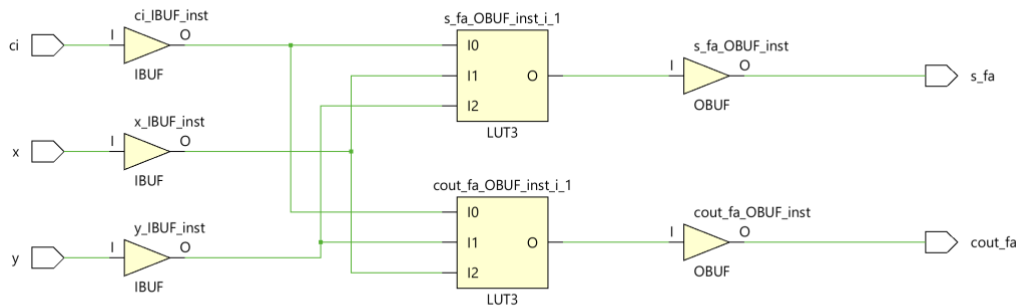













## How many luts.

Hierarchy		
Name	Slice LUTs (63400)	Bonded IOB (210)
FA	1	5

## Delay of circuit

gn Runs | Power | DRC | Timing ×

Q Combinational Delays

From Port	To Port	Max Delay	Max Process Corner	Min Delay	Min Process Corner
 ci	 cout_fa	5.557	SLOW	2.080	FAST
 ci	 s_fa	5.358	SLOW	2.002	FAST
 x	 cout_fa	5.671	SLOW	2.131	FAST
 x	 s_fa	5.462	SLOW	2.053	FAST
 y	 cout_fa	5.580	SLOW	2.099	FAST
 y	 s_fa	5.370	SLOW	2.022	FAST

## Comments:

We did full adder with 2 half adders. Full adder is different from half adder in input number. Full adder has 3 inputs but it does the same thing that adding.

## RIPPLE CARRY ADDER

Verilog code


```
module RCA(cout,s,x,y,ci);
    input [3:0]x;
    input [3:0]y;
    input ci;
    output cout;
    output [3:0]s;
    wire cout_rca_1,cout_rca_2,cout_rca_3;

    FA FA1 (cout_rca_1,s[0],x[0],y[0],ci);
    FA FA2 (cout_rca_2,s[1],x[1],y[1],cout_rca_1);
```


Test code

```
module tb_rca( );
    wire [3:0]sum; wire carry_out;
    reg [3:0]a, b; reg c;
    RCA uut(.x(a), .y(b), .ci(c), .s_rca(sum), .cout_rca(carry_out));
    initial begin
        a = 4'b0000; b = 4'b0000; c = 1'b0;
        #10; a = 4'b0000; b = 4'b0000; c = 1'b1;
        #10; a = 4'b0001; b = 4'b0001; c = 1'b0;
        #10; a = 4'b0001; b = 4'b0001; c = 1'b1;
        #10; a = 4'b0010; b = 4'b0010; c = 1'b0;
        #10; a = 4'b0010; b = 4'b0010; c = 1'b1;
        #10; a = 4'b0011; b = 4'b0011; c = 1'b0;
        #10; a = 4'b0011; b = 4'b0011; c = 1'b1;
        #10; a = 4'b0100; b = 4'b0100; c = 1'b0;
        #10; a = 4'b0100; b = 4'b0100; c = 1'b1;
        #10; a = 4'b0101; b = 4'b0101; c = 1'b0;
        #10; a = 4'b0101; b = 4'b0101; c = 1'b1;
        #10; a = 4'b0110; b = 4'b0110; c = 1'b0;
        #10; a = 4'b0110; b = 4'b0110; c = 1'b1;
        #10; a = 4'b0111; b = 4'b0111; c = 1'b0;
        #10; a = 4'b0111; b = 4'b0111; c = 1'b1;
        #10; a = 4'b1000; b = 4'b1000; c = 1'b0;
        #10; a = 4'b1000; b = 4'b1000; c = 1'b1;
        #10; a = 4'b1001; b = 4'b1001; c = 1'b0;
        #10; a = 4'b1001; b = 4'b1001; c = 1'b1;
        #10; a = 4'b1010; b = 4'b1010; c = 1'b0;
        #10; a = 4'b1010; b = 4'b1010; c = 1'b1;
        #10; a = 4'b1011; b = 4'b1011; c = 1'b0;
        #10; a = 4'b1011; b = 4'b1011; c = 1'b1;
        #10; a = 4'b1100; b = 4'b1100; c = 1'b0;
        #10; a = 4'b1100; b = 4'b1100; c = 1'b1;
```

## Rtl schema

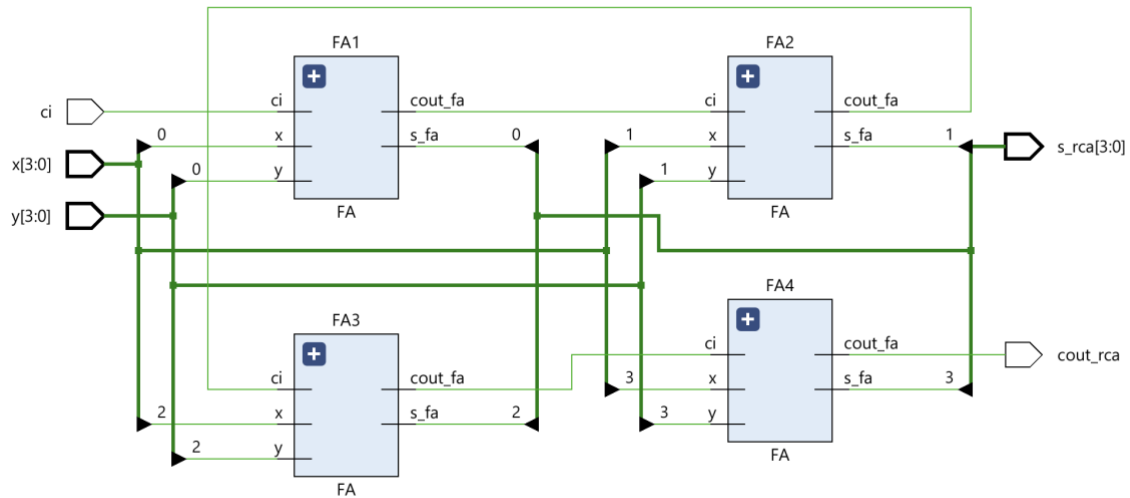

## Technology schema

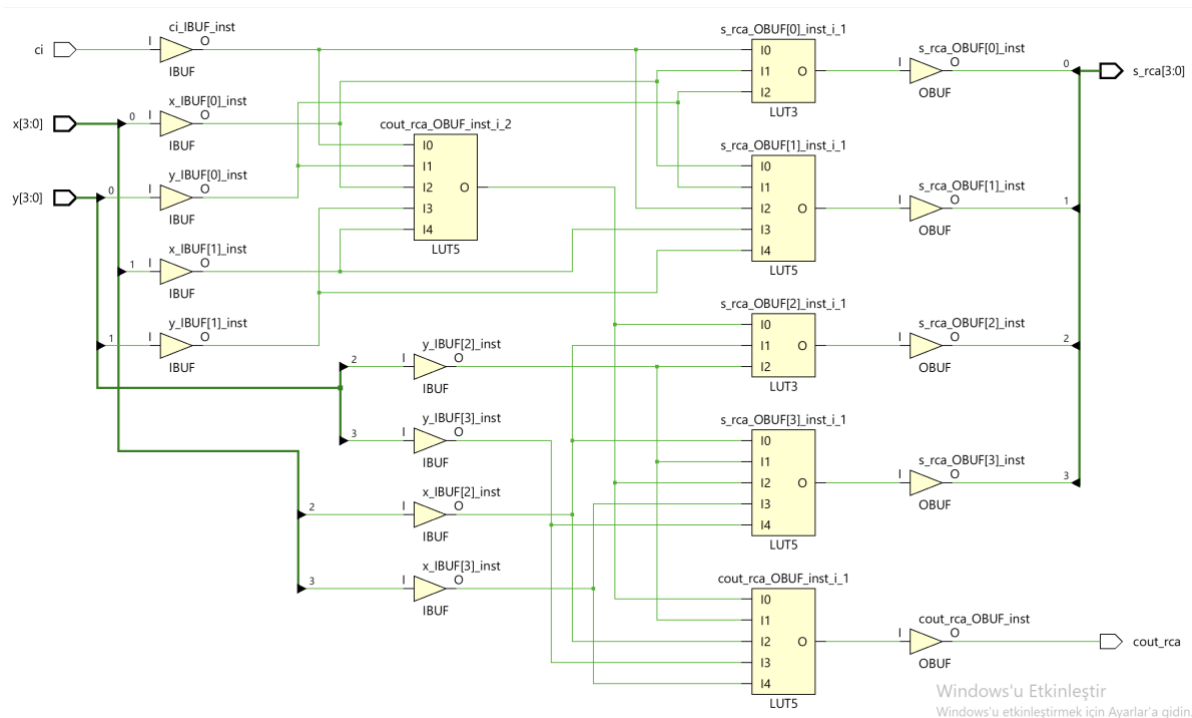

## How many luts

4

## Delay of circuit

Combinational Delays					
From Port	To Port	Max Delay	Max Process Corner	Min Delay	Min Process Corner
ci	cout_rca	4.923	SLOW	2.084	FAST
ci	s_rca[0]	4.512	SLOW	1.905	FAST
ci	s_rca[1]	4.526	SLOW	1.906	FAST
ci	s_rca[2]	4.923	SLOW	2.084	FAST
ci	s_rca[3]	4.926	SLOW	2.086	FAST
x[0]	cout_rca	4.923	SLOW	2.084	FAST
x[0]	s_rca[0]	4.512	SLOW	1.905	FAST
x[0]	s_rca[1]	4.522	SLOW	1.908	FAST
x[0]	s_rca[2]	4.923	SLOW	2.084	FAST
x[0]	s_rca[3]	4.926	SLOW	2.086	FAST
x[1]	cout_rca	4.923	SLOW	2.084	FAST
x[1]	s_rca[1]	4.524	SLOW	1.907	FAST
x[1]	s_rca[2]	4.923	SLOW	2.084	FAST
x[1]	s_rca[3]	4.926	SLOW	2.086	FAST
x[2]	cout_rca	4.512	SLOW	1.905	FAST
x[2]	s_rca[2]	4.512	SLOW	1.905	FAST
x[2]	s_rca[3]	4.522	SLOW	1.908	FAST
x[3]	cout_rca	4.512	SLOW	1.905	FAST
x[3]	s_rca[3]	4.526	SLOW	1.906	FAST
y[0]	cout_rca	4.923	SLOW	2.084	FAST
y[0]	s_rca[0]	4.512	SLOW	1.905	FAST
y[0]	s_rca[1]	4.523	SLOW	1.908	FAST
y[0]	s_rca[2]	4.923	SLOW	2.084	FAST
y[0]	s_rca[3]	4.926	SLOW	2.086	FAST
y[1]	cout_rca	4.923	SLOW	2.084	FAST
y[1]	s_rca[1]	4.515	SLOW	1.907	FAST
y[1]	s_rca[2]	4.923	SLOW	2.084	FAST
y[1]	s_rca[3]	4.926	SLOW	2.086	FAST
y[2]	cout_rca	4.512	SLOW	1.905	FAST
y[2]	s_rca[2]	4.512	SLOW	1.905	FAST
y[2]	s_rca[3]	4.523	SLOW	1.908	FAST
y[3]	cout_rca	4.512	SLOW	1.905	FAST
y[3]	s_rca[3]	4.524	SLOW	1.907	FAST

**Comments:** rca is adder different from previous adders. Use full adder for that. In rca adding process output of full adder is input of other full adder input. So this have pros. And cos. We can understand system easily but system using more component



## RIPPLE CARY ADDER WITH “GENERATE-FOR”

### Verilog code


```
module parametric_RCA(cout,s,x,y,cin);
    parameter SIZE=4;
    input [SIZE-1:0] x, y;
    input cin;
    output cout;
    output [SIZE-1:0]s;
    wire [SIZE-1:1] cout_rca_;
    FA FAa (cout_rca_[1],s[0],x[0],y[0],cin);
    genvar i;
    generate for (i=2;i<SIZE;i=i+1)
    begin

        FA FAb (cout_rca_[i],s[i-1],x[i-1],y[i-1],cout_rca_[i-1]);
    end
endmodule
```


### Test code

```
module tb_param_rca( );
    wire [3:0]sum; wire carry_out;
    reg [3:0]a, b; reg c;
    parametric_RCA uut(.x(a), .y(b), .cin(c), .s_rca(sum), .cout_rca(carry_out));
    initial
    begin
        a = 4'b0000; b = 4'b0000; c = 1'b0;
        #10;
        a = 4'b0000; b = 4'b0000; c = 1'b1;
        #10;
        a = 4'b0001; b = 4'b0001; c = 1'b0;
        #10;
        a = 4'b0001; b = 4'b0001; c = 1'b1;
        #10;
        a = 4'b0010; b = 4'b0010; c = 1'b0;
        #10;
        a = 4'b0010; b = 4'b0010; c = 1'b1;
        #10;
        a = 4'b0011; b = 4'b0011; c = 1'b0;
        #10;
        a = 4'b0011; b = 4'b0011; c = 1'b1;
        #10;
        a = 4'b0100; b = 4'b0100; c = 1'b0;
        #10;
        a = 4'b0100; b = 4'b0100; c = 1'b1;
    end
endmodule
```


## Testbench simulation for 4-bits

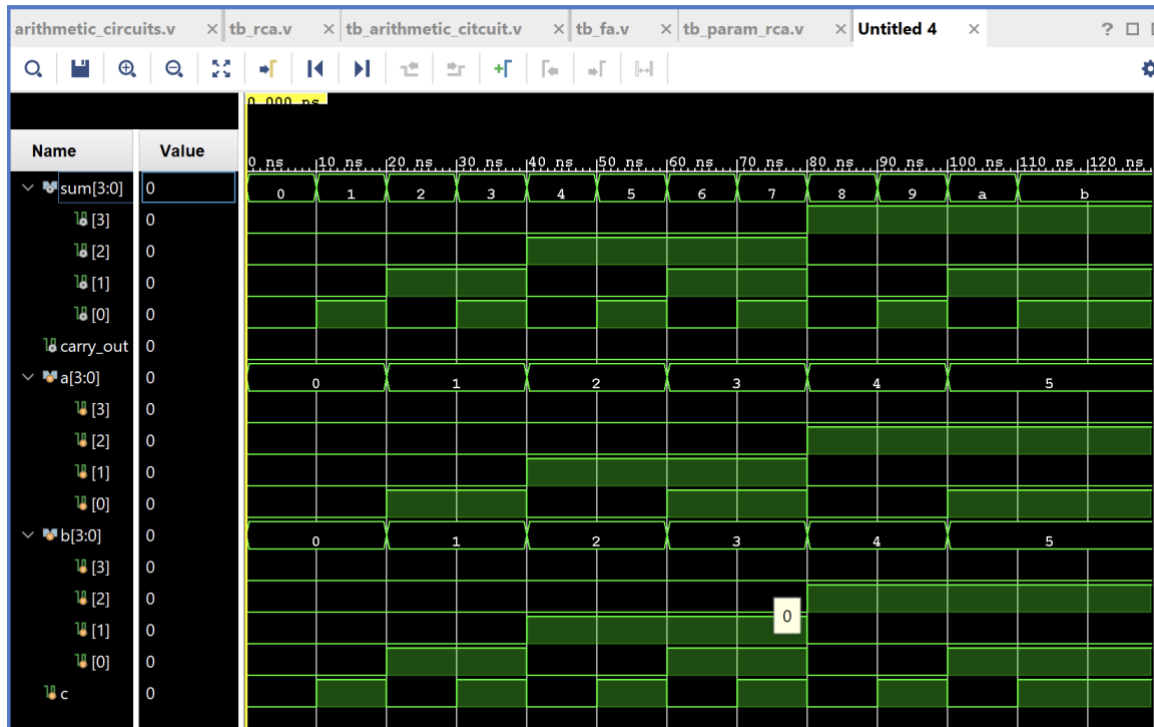


## Testbench simulation for 8-bits

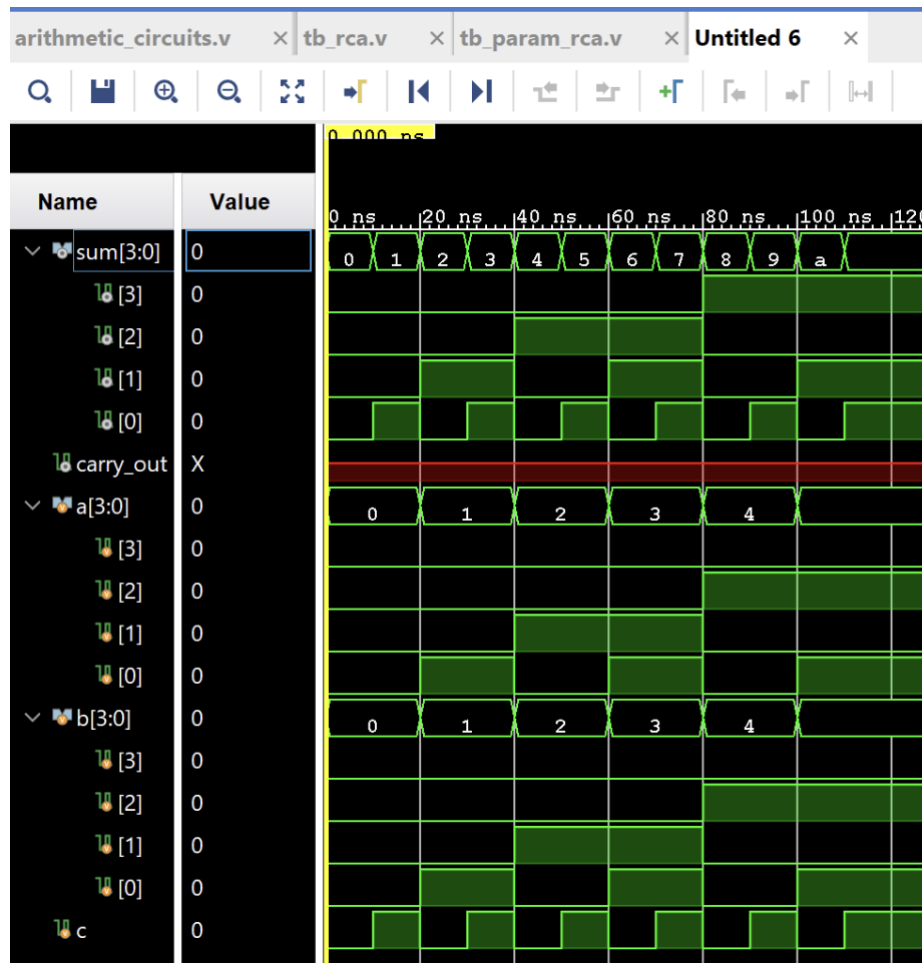

## Rtl schema

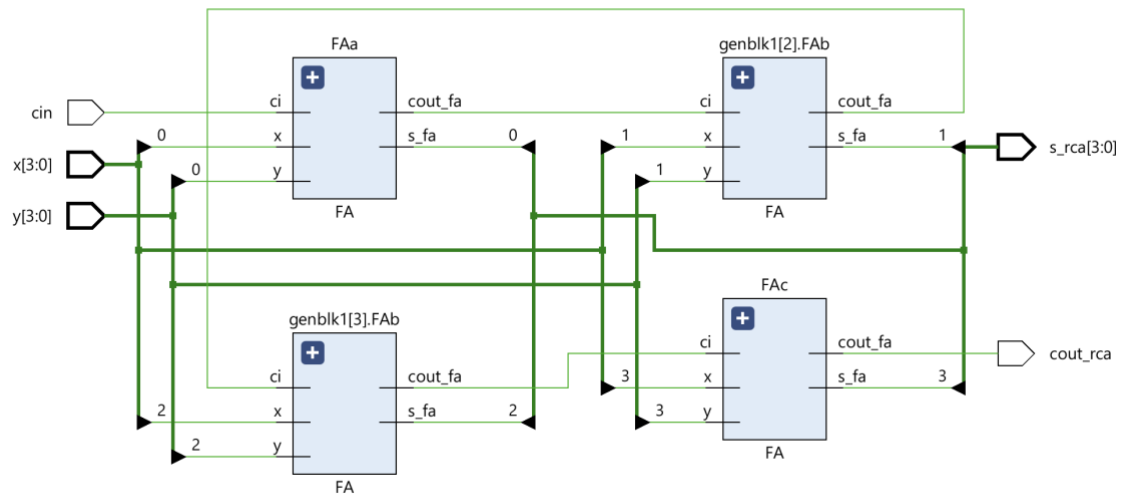

## Technology schema

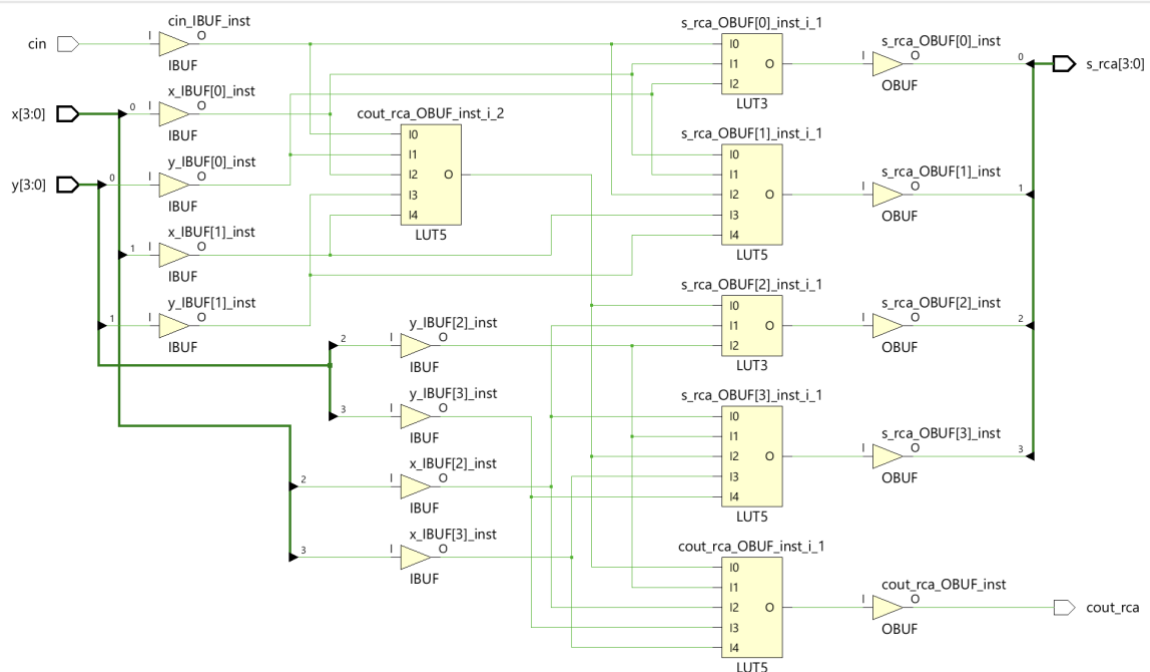

## How many luts

Hierarchy		
Name	Slice LUTs (63400)	Bonded IOB (210)
parametric_RCA	4	14

## 4-bit schematic Compare 4-bit rca

these are doing same thing . there are there are not differences. Luts number are same rtl and technology schema are same. But writing code is different.

## CARRY LOOKAHEAD ADDER

### Verilog code

```
module CLA (cout,s,x,y,c0);
    input [3:0] x,y;
    input c0;
    output cout;
    output [3:0]s;
    wire [3:0] G,P;
    wire [3:0] C;

    assign G[0] = x[0] & y[0];
    assign G[1] = x[1] & y[1];
    assign G[2] = x[2] & y[2];
    assign G[3] = x[3] & y[3];

    assign P[0] = x[0] ^ y[0];
    assign P[1] = x[1] ^ y[1];
    assign P[2] = x[2] ^ y[2];
    assign P[3] = x[3] ^ y[3];
    assign C[0] = G[0] | (P[0] & c0);
    assign C[1] = G[1] | (P[1] & C[0]);
    assign C[2] = G[2] | (P[2] & C[1]);
    assign C[3] = G[3] | (P[3] & C[2]);
    assign s[0]= P[0] ^ c0;
```

## Test code

```


module tb_cla();
    reg [3:0]x,y;
    reg c0;
    wire [3:0]s_cla;
    wire cout_cla;
    CLA uut(.x(x),.y(y),c0(c0),cout_cla(cout_cla),s_cla(s_cla));

    initial begin


        x= 4'd0; y=4'd0; c0=0;
        #10
        x= 4'd1; y=4'd1; c0=0;
        #10
        x= 4'd2; y=4'd2; c0=0;
        #10
        x= 4'd4; y=4'd3; c0=0;
    end

```

## Rtl schema

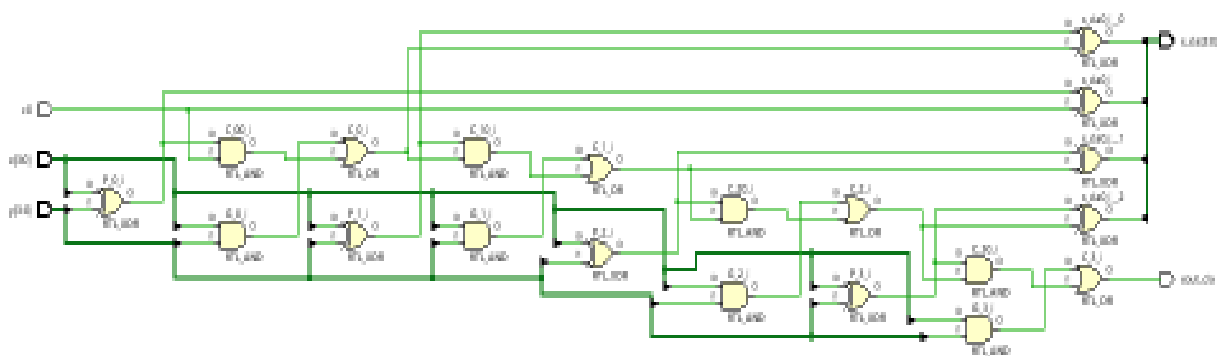

## Technology schema

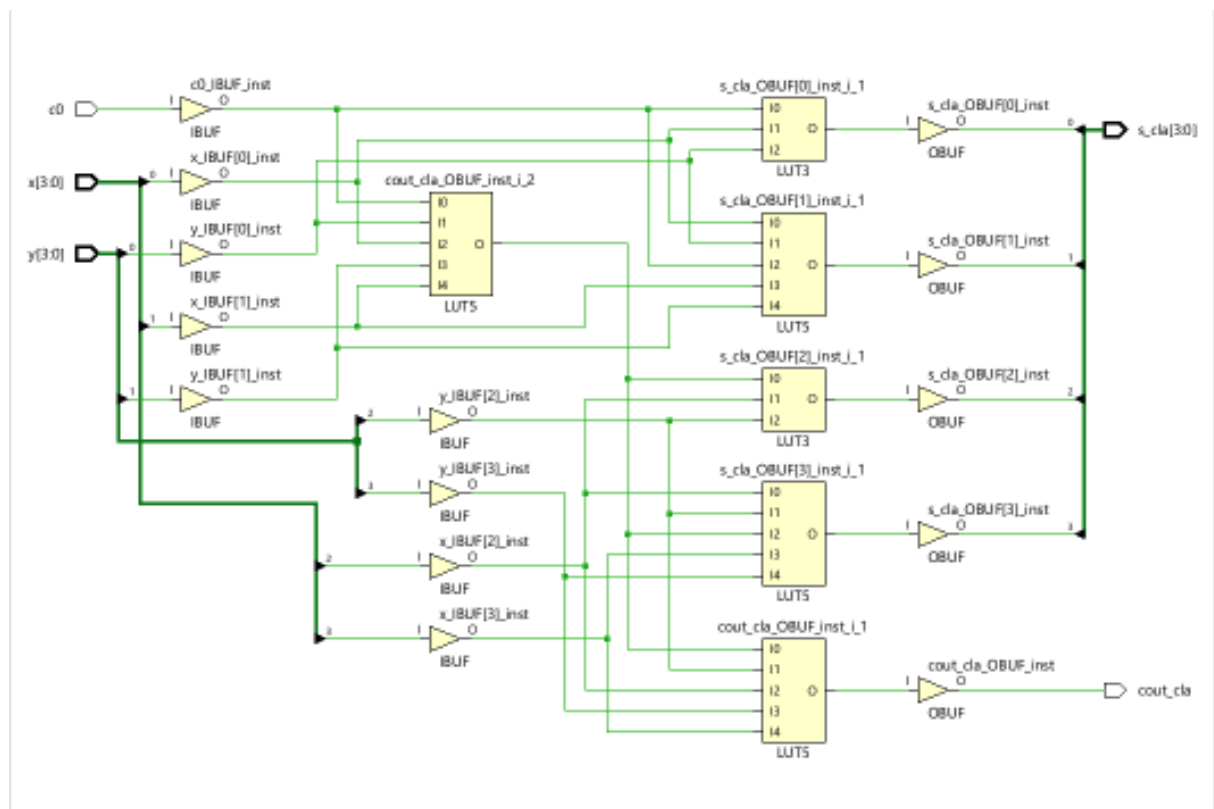

## How many luts

Hierarchy			
Name	^1	Slice LUTs (63400)	Bonded IOB (210)
CLA		4	14

## Delay of circuit

Combinational Delays						
From Port	To Port	Max Delay	Max Process Corner	Min Delay	Min Process Corner	
c0	cout_cla	6.287	SLOW	2.433	FAST	
c0	s_cla[0]	5.546	SLOW	2.115	FAST	
c0	s_cla[1]	5.926	SLOW	2.254	FAST	
c0	s_cla[2]	6.312	SLOW	2.445	FAST	
c0	s_cla[3]	6.066	SLOW	2.350	FAST	
x[0]	cout_cla	6.039	SLOW	2.346	FAST	
x[0]	s_cla[0]	5.944	SLOW	2.294	FAST	
x[0]	s_cla[1]	5.671	SLOW	2.166	FAST	
x[0]	s_cla[2]	6.064	SLOW	2.358	FAST	
x[0]	s_cla[3]	5.818	SLOW	2.263	FAST	
x[1]	cout_cla	6.288	SLOW	2.447	FAST	
x[1]	s_cla[1]	5.928	SLOW	2.268	FAST	
x[1]	s_cla[2]	6.313	SLOW	2.459	FAST	
x[1]	s_cla[3]	6.067	SLOW	2.364	FAST	
x[2]	cout_cla	5.885	SLOW	2.265	FAST	
x[2]	s_cla[2]	5.476	SLOW	2.116	FAST	
x[2]	s_cla[3]	5.657	SLOW	2.182	FAST	
x[3]	cout_cla	6.090	SLOW	2.375	FAST	
x[3]	s_cla[3]	5.863	SLOW	2.292	FAST	
y[0]	cout_cla	6.161	SLOW	2.372	FAST	
y[0]	s_cla[0]	5.723	SLOW	2.188	FAST	
y[0]	s_cla[1]	5.803	SLOW	2.191	FAST	
y[0]	s_cla[2]	6.187	SLOW	2.383	FAST	
y[0]	s_cla[3]	5.940	SLOW	2.289	FAST	
y[1]	cout_cla	6.084	SLOW	2.339	FAST	
y[1]	s_cla[1]	5.728	SLOW	2.157	FAST	
y[1]	s_cla[2]	6.110	SLOW	2.350	FAST	
y[1]	s_cla[3]	5.864	SLOW	2.256	FAST	
y[2]	cout_cla	5.918	SLOW	2.268	FAST	
y[2]	s_cla[2]	5.715	SLOW	2.181	FAST	
y[2]	s_cla[3]	5.691	SLOW	2.185	FAST	
y[3]	cout_cla	5.663	SLOW	2.144	FAST	
y[3]	s_cla[3]	5.434	SLOW	2.064	FAST	

**Comments:** cla is 4 bit adder. Doing same thing previous. But its working fast and not using more components. But in bigger system that cause decreasing understandable. It will more confusing

## ADDER-SUBTRACTOR CIRCUIT

### Verilog code

```
module Add_Sub (
    input [3:0]A,
    input [3:0]B,
    input ci,
    output [3:0]s,
    output cout,
    output V
);
    wire [3:0] c_fa;
    wire [3:0] i_fa;
    assign i_fa[0]=B[0] ^ ci ;
    assign i_fa[1]=B[1] ^ ci ;
    assign i_fa[2]=B[2] ^ ci ;
    assign i_fa[3]=B[3] ^ ci ;
    FA FA5 (c_fa[0],s[0],A[0],i_fa[0],ci);
    FA FA6 (c_fa[1],s[1],A[1],i_fa[1],c_fa[0]);
```


### Test code

```
module tb_Add_Sub();
    reg[3:0]A,B;
    reg ci;
    wire cout;
    wire [3:0]s;
    wire V;
    Add_Sub UUT(.A(A),.B(B),.ci(ci),.cout(cout),.s(s),.V(V) );


    initial begin
        A=4'd0; B=4'd0; ci=1'b0;
        #10; A=4'd10; B=4'd1;
        #10; A=4'd7; B=4'd14;
        #10; A=4'd6; B=4'd5;
        #10; A=4'd2; B=4'd8;
        #10; A=4'd11; B=4'd11;
        #10; A=4'd3; B=4'd9;
        #10; A=4'd15; B=4'd15;
        #10; A=4'd0; B=4'd0; ci=1'b1;
        #10; A=4'd7; B=4'd14;
        #10; A=4'd6; B=4'd5;
        #10; A=4'd2; B=4'd8;
        #10; A=4'd11; B=4'd11;
```



## Rtl schema

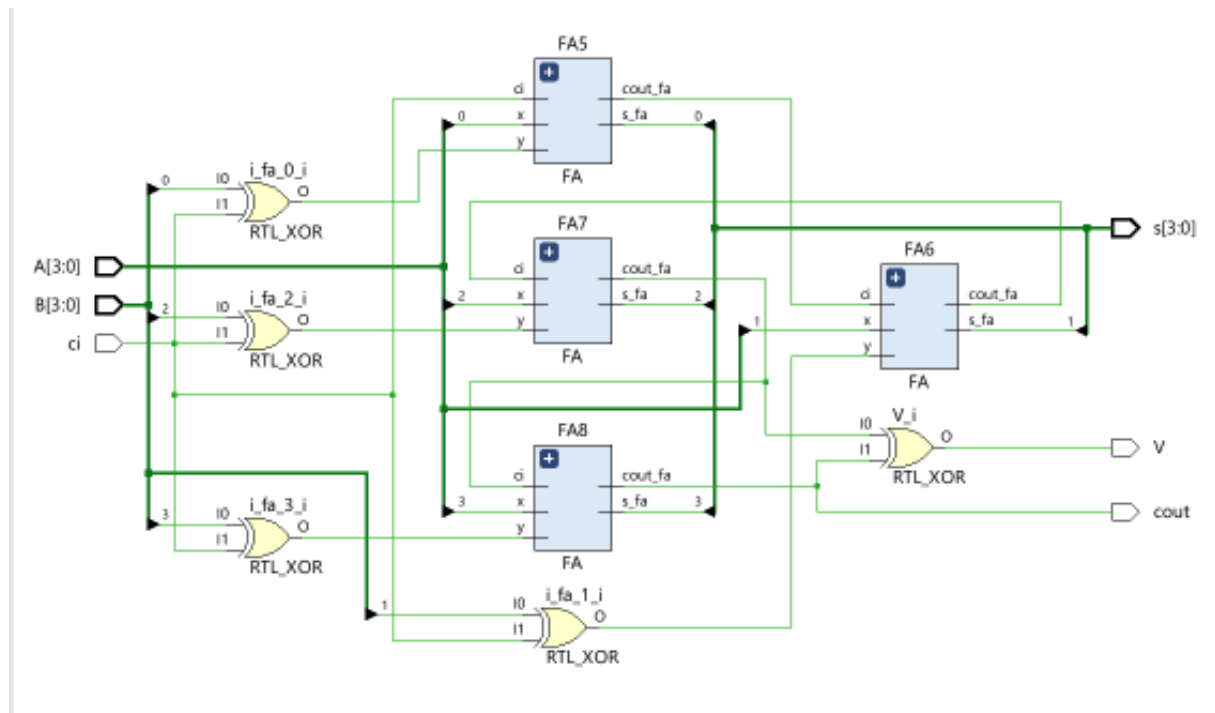

## Technology schema

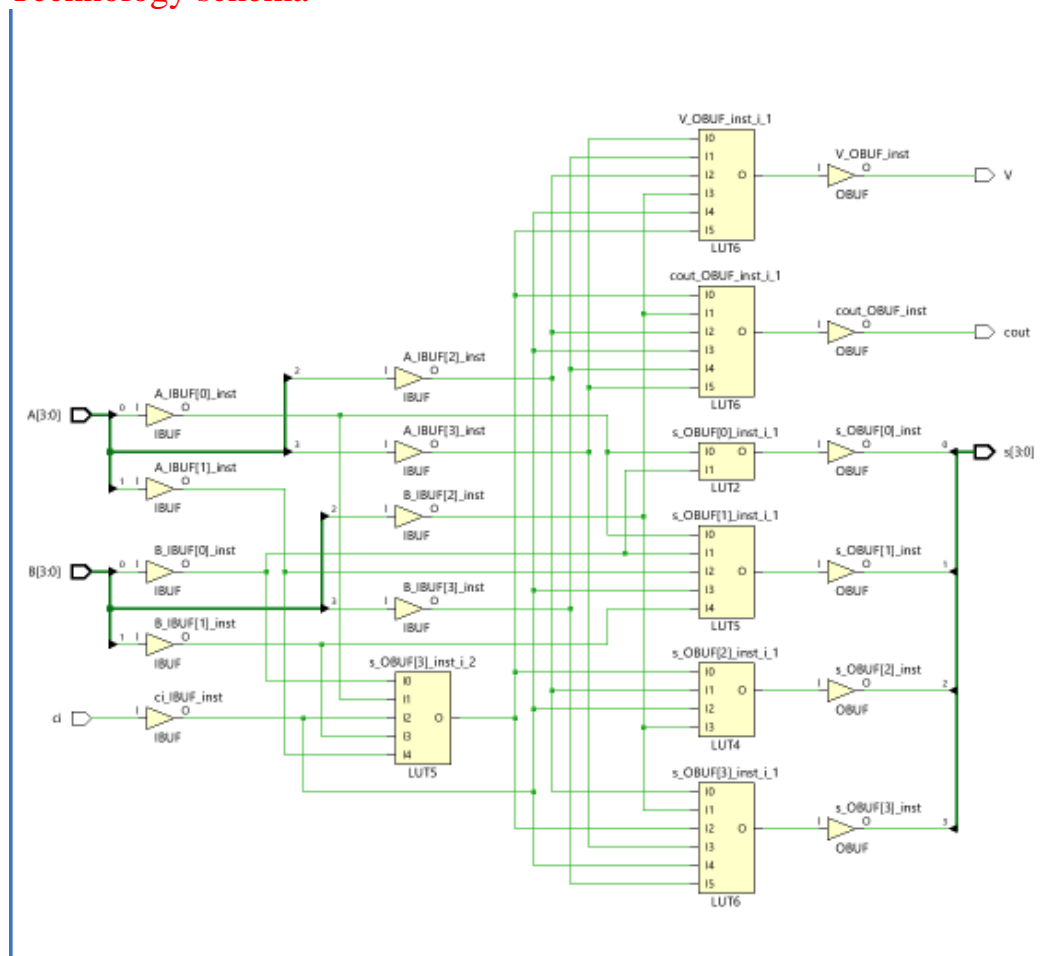

How many luts.

Name	Slice LUTs (63400)	Bonded IOB (210)
Add_Sub	6	15

Delay of circuit

IMPLEMENTED DESIGN - xc7k70tfbv676-1 (active)							
Tcl Console	Messages	Log	Reports	Design Runs	Power	DRC	Timing x
Combinational Delays							
General Information	From Port	To Port	Max Delay	Max Process Corner	Min Delay	Min Process Corner	
Timer Settings	A[0]	V	9.088	SLOW	3.480	FAST	
Design Timing Summary	A[0]	cout	7.026	SLOW	2.873	FAST	
> Check Timing (0)	A[0]	s[0]	8.369	SLOW	3.191	FAST	
Intra-Clock Paths	A[0]	s[1]	10.388	SLOW	4.236	FAST	
Inter-Clock Paths	A[0]	s[2]	9.557	SLOW	3.630	FAST	
Other Path Groups	A[0]	s[3]	7.010	SLOW	2.866	FAST	
User Ignored Paths	A[1]	V	8.364	SLOW	3.151	FAST	
> Unconstrained Paths	A[1]	cout	6.302	SLOW	2.544	FAST	
▼ Datasheet	A[1]	s[1]	9.656	SLOW	3.906	FAST	
Input Ports Setup/Hold	A[1]	s[2]	8.834	SLOW	3.302	FAST	
Output Ports Clock-to-out	A[1]	s[3]	6.286	SLOW	2.537	FAST	
Combinational Delays	A[2]	V	9.317	SLOW	3.527	FAST	
Setup between Clocks	A[2]	cout	7.657	SLOW	3.069	FAST	
	A[2]	s[2]	10.382	SLOW	3.903	FAST	
	A[2]	s[3]	7.643	SLOW	3.062	FAST	
	A[3]	V	7.959	SLOW	2.960	FAST	
	A[3]	cout	5.929	SLOW	2.352	FAST	
	A[3]	s[3]	5.913	SLOW	2.346	FAST	
	B[0]	V	6.660	SLOW	2.647	FAST	
	B[0]	cout	4.598	SLOW	2.039	FAST	
	B[0]	s[0]	5.538	SLOW	2.128	FAST	
	B[0]	s[1]	7.959	SLOW	3.403	FAST	
	B[0]	s[2]	7.130	SLOW	2.797	FAST	
	B[0]	s[3]	4.582	SLOW	2.033	FAST	
	B[1]	V	8.473	SLOW	3.183	FAST	
	B[1]	cout	6.410	SLOW	2.576	FAST	
	B[1]	s[1]	9.775	SLOW	3.937	FAST	
	B[1]	s[2]	8.942	SLOW	3.333	FAST	
	B[1]	s[3]	6.395	SLOW	2.569	FAST	
	B[2]	V	7.626	SLOW	2.828	FAST	
	B[2]	cout	5.823	SLOW	2.328	FAST	
	B[2]	s[2]	8.405	SLOW	3.108	FAST	
	B[2]	s[3]	5.812	SLOW	2.323	FAST	
	B[3]	V	7.494	SLOW	2.777	FAST	
	B[3]	cout	5.575	SLOW	2.222	FAST	
	B[3]	s[3]	5.565	SLOW	2.218	FAST	
	ci	V	8.610	SLOW	2.915	FAST	
	ci	cout	6.547	SLOW	2.265	FAST	
	ci	s[1]	9.910	SLOW	4.002	FAST	
	ci	s[2]	9.079	SLOW	3.251	FAST	
	ci	s[3]	6.532	SLOW	2.258	FAST	

## Comments

Adder and subtractor device do adder ci of doing subtractor when ci input is on. In output there are sum count and V. V is overflow sign.