



# DIGITAL SYSTEM DESIGN APPLICATION PROJECT 2

İBRAHİM SAMED YALÇIN

040180055

```
`timescale 1ns / 1ps

module MSI_Library(

);
endmodule

module DECODER(
input [3:0] IN,
output reg [15:0] O
);

always @(IN) begin

    case(IN)
        4'h0 : O = 16'b0000_0000_0000_0001;
        4'h1 : O = 16'b0000_0000_0000_0010;
        4'h2 : O = 16'b0000_0000_0000_0100;
        4'h3 : O = 16'b0000_0000_0000_1000;
        4'h4 : O = 16'b0000_0000_0001_0000;
        4'h5 : O = 16'b0000_0000_0010_0000;
        4'h6 : O = 16'b0000_0000_0100_0000;
        4'h7 : O = 16'b0000_0000_1000_0000;
        4'h8 : O = 16'b0000_0001_0000_0000;
        4'h9 : O = 16'b0000_0010_0000_0000;
        4'hA : O = 16'b0000_0100_0000_0000;
        4'hB : O = 16'b0000_1000_0000_0000;
        4'hC : O = 16'b0001_0000_0000_0000;
        4'hD : O = 16'b0010_0000_0000_0000;
        4'hE : O = 16'b0100_0000_0000_0000;
        4'hF : O = 16'b1000_0000_0000_0000;

        default : O=16'd0;
    endcase
end
endmodule
```

DECODER

MSI LIBRARY

## TOP MODULE

```
`timescale 1ns / 1ps

module top_module(
    input [7:0] sw,
    input [3:0] btn,
    output [7:0] led,
    output [6:0] cat,
    output [3:0] an,
    output dp
);
    assign an = 4'b1110;
    wire [15:0] new;
    assign dp = new[15];
    assign cat = new[14:8];
    assign led = new[7:0];

    DECODER decoder1(.IN(sw[3:0]),.O(new));

    //ENCODER encoder (.IN(sw[3:0]),.O(led[1:0]),.V(led[7]));
```

TEST BENCH

```

`timescale 1ns / 1ps
module top_module_tb(
);
    reg [7:0] sw;
    reg [3:0] btn;
    wire [7:0] led;
    wire [6:0] cat;
    wire [3:0] an;
    wire dp;

    top_module uut(sw,btn,led,cat,an,dp);


    initial
    begin
        //decoder
        sw=4'd0;
        #10; sw=4'd1;
        #10; sw=4'd2;
        #10; sw=4'd3;
        #10; sw=4'd4;
        #10; sw=4'd5;
        #10; sw=4'd6;
        #10; sw=4'd7;
        #10; sw=4'd8;
        #10; sw=4'd9;
        #10; sw=4'd10;
        #10; sw=4'd11;
        #10; sw=4'd12;
        #10; sw=4'd13;
        #10; sw=4'd14;
        #10; sw=4'd15;
        #10;

        $finish;
    end
endmodule


```

BEHAVIORAL

SCHEMATIC

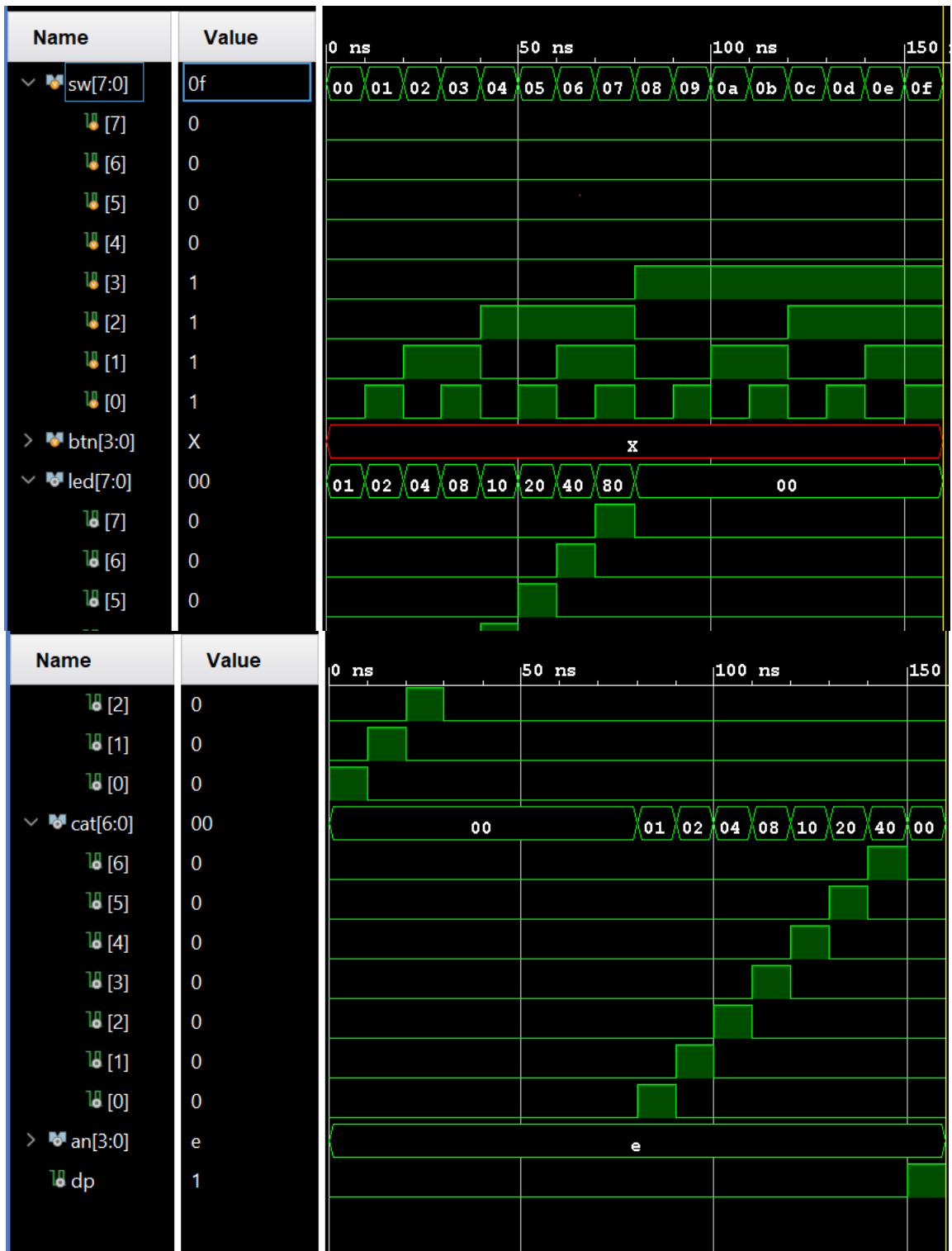


RTL SHEMA

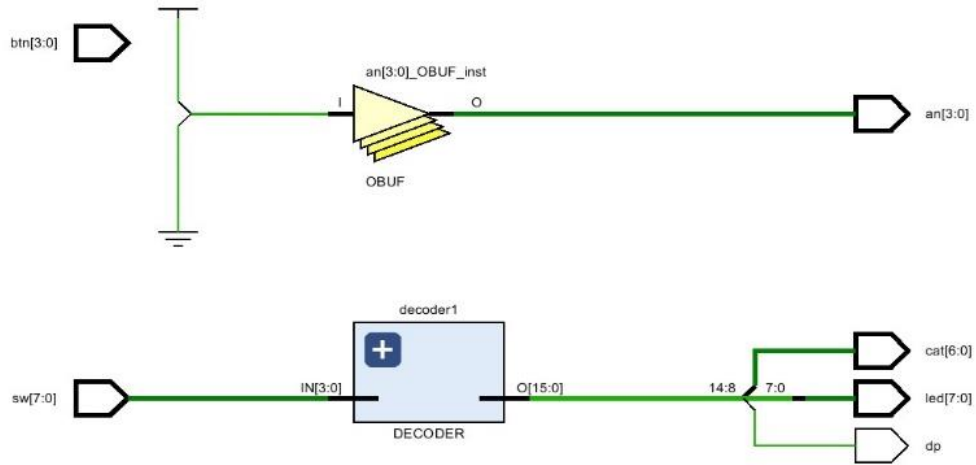

TECHNOLOGIC SHEMA



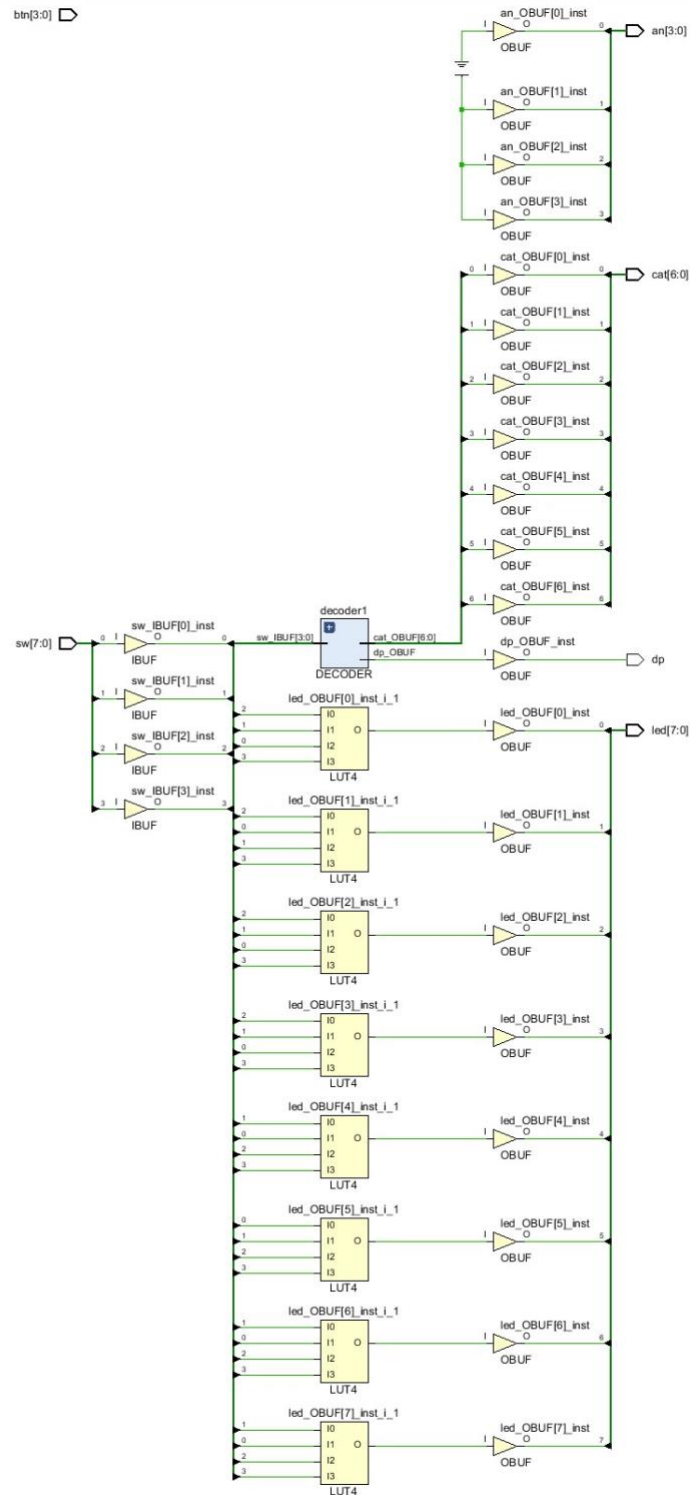

THERE ARE 8 LUTS

DELAY:

From Port	To Port	Max Delay	Max Process Corner	Min Delay	Min Process Corner
sw[0]	cat[0]	7.484	SLOW	2.560	FAST
sw[0]	cat[1]	7.852	SLOW	2.688	FAST
sw[0]	cat[2]	7.054	SLOW	2.400	FAST
sw[0]	cat[3]	7.019	SLOW	2.360	FAST
sw[0]	cat[4]	7.551	SLOW	2.556	FAST
sw[0]	cat[5]	7.017	SLOW	2.360	FAST
sw[0]	cat[6]	7.526	SLOW	2.528	FAST
sw[0]	dp	7.146	SLOW	2.352	FAST
sw[0]	led[0]	7.671	SLOW	2.661	FAST
sw[0]	led[1]	7.800	SLOW	2.727	FAST
sw[0]	led[2]	8.071	SLOW	2.798	FAST
sw[0]	led[3]	7.623	SLOW	2.609	FAST
sw[0]	led[4]	7.237	SLOW	2.499	FAST
sw[0]	led[5]	7.451	SLOW	2.569	FAST
sw[0]	led[6]	7.692	SLOW	2.623	FAST
sw[0]	led[7]	8.022	SLOW	2.757	FAST
sw[1]	cat[0]	7.469	SLOW	2.588	FAST
sw[1]	cat[1]	7.834	SLOW	2.714	FAST
sw[1]	cat[2]	7.035	SLOW	2.427	FAST
sw[1]	cat[3]	6.916	SLOW	2.356	FAST
sw[1]	cat[4]	7.530	SLOW	2.581	FAST
sw[1]	cat[5]	6.715	SLOW	2.278	FAST
sw[1]	cat[6]	7.222	SLOW	2.444	FAST
sw[1]	dp	7.041	SLOW	2.346	FAST
sw[1]	led[0]	8.209	SLOW	2.853	FAST
sw[1]	led[1]	7.778	SLOW	2.747	FAST
sw[1]	led[2]	8.047	SLOW	2.816	FAST
sw[1]	led[3]	7.601	SLOW	2.628	FAST
sw[1]	led[4]	7.742	SLOW	2.697	FAST
sw[1]	led[5]	7.737	SLOW	2.701	FAST
sw[1]	led[6]	7.977	SLOW	2.758	FAST
sw[1]	led[7]	8.000	SLOW	2.774	FAST
sw[2]	cat[0]	7.383	SLOW	2.563	FAST
sw[2]	cat[1]	7.716	SLOW	2.695	FAST
sw[2]	cat[2]	6.949	SLOW	2.402	FAST
sw[2]	cat[3]	7.158	SLOW	2.440	FAST
sw[2]	cat[4]	7.412	SLOW	2.563	FAST
sw[2]	cat[5]	6.629	SLOW	2.253	FAST
sw[2]	cat[6]	7.104	SLOW	2.425	FAST
sw[2]	dp	7.285	SLOW	2.432	FAST
sw[2]	led[0]	8.532	SLOW	2.966	FAST
sw[2]	led[1]	7.838	SLOW	2.778	FAST
sw[2]	led[2]	8.075	SLOW	2.853	FAST
sw[2]	led[3]	7.673	SLOW	2.671	FAST
sw[2]	led[4]	8.064	SLOW	2.811	FAST
sw[2]	led[5]	8.064	SLOW	2.819	FAST
sw[2]	led[6]	8.305	SLOW	2.875	FAST
sw[2]	led[7]	8.039	SLOW	2.823	FAST
sw[3]	cat[0]	7.659	SLOW	2.645	FAST
sw[3]	cat[1]	8.024	SLOW	2.775	FAST
sw[3]	cat[2]	7.225	SLOW	2.484	FAST
sw[3]	cat[3]	6.656	SLOW	2.252	FAST
sw[3]	cat[4]	7.721	SLOW	2.642	FAST
sw[3]	cat[5]	6.905	SLOW	2.334	FAST
sw[3]	cat[6]	7.412	SLOW	2.504	FAST
sw[3]	dp	6.748	SLOW	2.248	FAST
sw[3]	led[0]	8.689	SLOW	3.014	FAST
sw[3]	led[1]	7.968	SLOW	2.804	FAST
sw[3]	led[2]	8.237	SLOW	2.876	FAST
sw[3]	led[3]	7.788	SLOW	2.686	FAST
sw[3]	led[4]	8.221	SLOW	2.860	FAST
sw[3]	led[5]	8.214	SLOW	2.863	FAST
sw[3]	led[6]	8.456	SLOW	2.919	FAST
sw[3]	led[7]	8.185	SLOW	2.834	FAST

ENCODER

## MSI LIBRARY

```
module ENCODER(  
  input [3:0] IN,  
  output [1:0] O,  
  output V );  
  wire x,y,z;  
  not (x,IN[2]);  
  and (y,x,IN[1]);  
  or (O[0],y,IN[3]);  
  or (O[1],IN[2],IN[3]);  
endmodule
```

## TOP MODULE

```

`timescale 1ns / 1ps

module top_module(
input [7:0] sw,
input [3:0] btn,
output [7:0] led,
output [6:0] cat,
output [3:0] an,
output dp
);

assign an =4'b1110;
wire [15:0] new;
assign dp = new[15];
assign cat = new[14:8];
assign led = new[7:0];

// DECODER decoder1(.IN(sw[3:0]),.O(new));

ENCODER encoder (.IN(sw[3:0]),.O(led[1:0]),.V(led[7]));
//MUX mux (.D(sw[3:0]),.S(btn[1:0]),.O(led[0]));
//DEMUX demux
(.S0(btn[0]),.D(sw[0]),.S1(btn[1]),.O(led[3:0]));
endmodule

```

## TESTSTBENCH

BEHAVIORAL

```

`timescale 1ns / 1ps
module top_module_tb(
);
    reg [7:0] sw;
    reg [3:0] btn;
    wire [7:0] led;
    wire [6:0] cat;
    wire [3:0] an;
    wire dp;


    top_module uut(sw,btn,led,cat,an,dp);


    initial
    begin
        /
        sw=4'd0;
        #10; sw=4'b0001;
        #10; sw=4'b0010;
        #10; sw=4'b0100;
        #10; sw=4'b1000;
        ;
        #10;

        $finish;
    end
/*


```

SHEMA

 


 

## RTL SHEMA

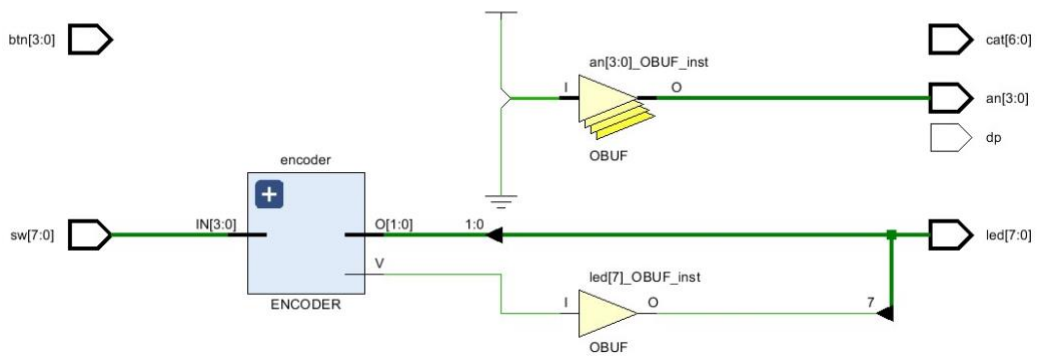


## TECHNOLOGIC SEHMA

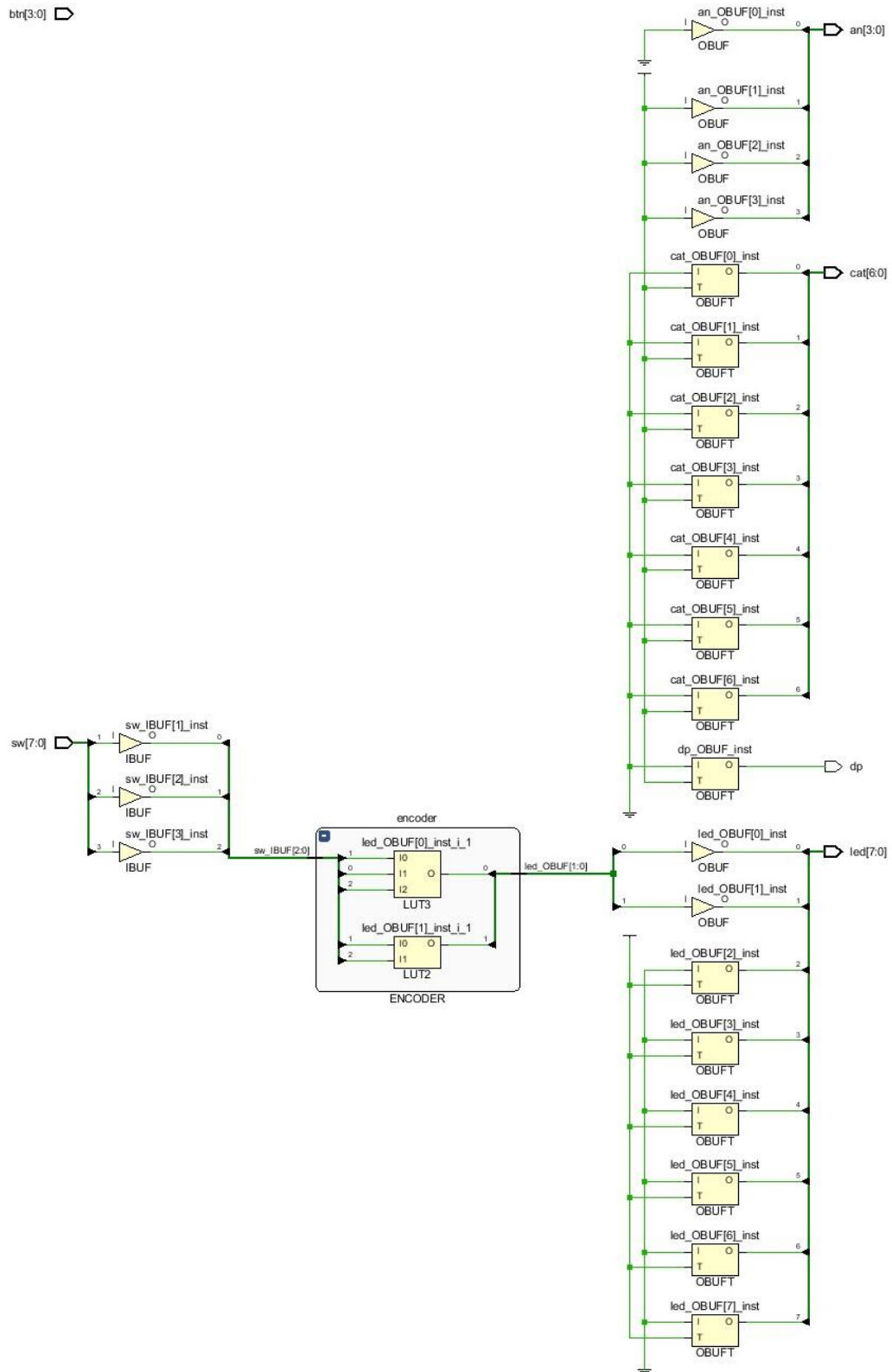

## TIMING DELAY REPORT

From Port	To Port	Max Delay	Max Process Corner	Min Delay	Min Process Corner
sw[1]	led[0]	7.102	SLOW	2.422	FAST
sw[2]	led[0]	7.523	SLOW	2.559	FAST
sw[2]	led[1]	7.274	SLOW	2.499	FAST
sw[3]	led[0]	7.690	SLOW	2.604	FAST
sw[3]	led[1]	7.439	SLOW	2.541	FAST

## UTILIZATION

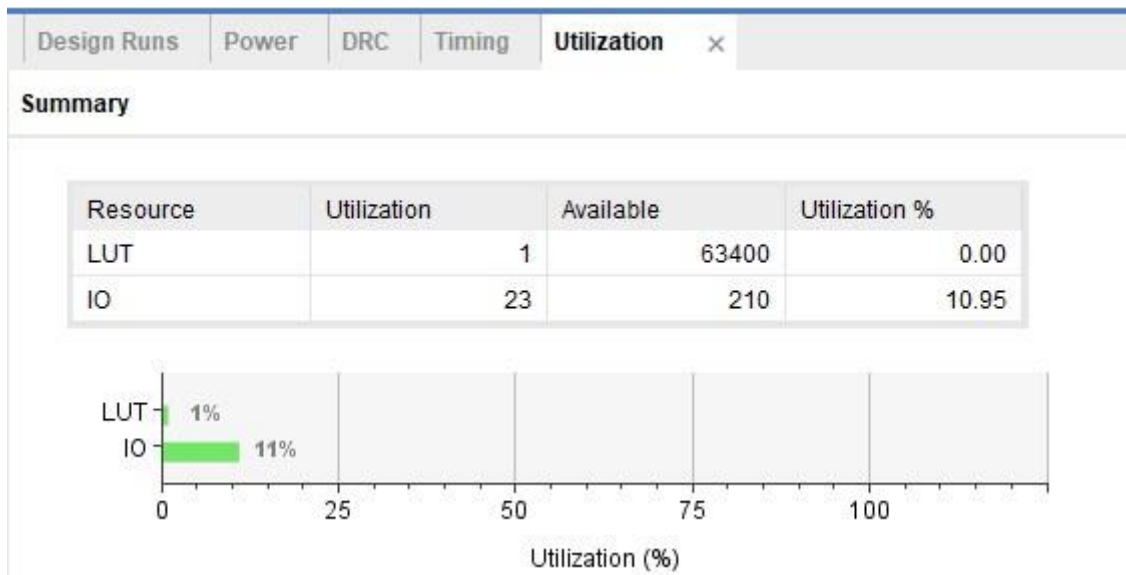



## MULTIPLEXER

### MSI LIBRARY

```

module MUX(
input wire [3:0] D,
input wire [1:0] S,
output O);
assign O = ((~S[1] & ~S[0] & D[0]) | (~S[1] & S[0] & D[1]) | (~S[0] & S[1] & D[2]) | (S[1] & S[0] & D[3]));
/*always@(S) begin
case(S)
2'b00 : O=D[0];
2'b01 : O=D[1];
2'b10 : O=D[2];
2'b11 : O=D[3];

endcase
end*/

```

### TOP MODULE

```

`timescale 1ns / 1ps

```

```

module top_module(
input [7:0] sw,
input [3:0] btn,
output [7:0] led,
output [6:0] cat,
output [3:0] an,
output dp
);

assign an =4'b1110;
wire [15:0] new;
assign dp = new[15];
assign cat = new[14:8];
assign led = new[7:0];

// DECODER decoder1(.IN(sw[3:0]),.O(new));

```

## TEST BENCH

```
top_module uut(sw,btn,led,cat,an,dp);
```

```
initial
```

```
begin
```

```
    //mux
```

```
    sw=4'd0; btn=2'd0;
```

```
    #10; sw=4'b0001;
```

```
    #10; sw=4'b0010;
```

```
    #10; sw=4'b0100;
```

```
    #10; sw=4'b1000;
```

```
    ;
```

```
    sw=4'd0; btn=2'd1;
```


```
    #10; sw=4'b0001;
```

```
    #10; sw=4'b0010;
```


```
    #10; sw=4'b0100;
```


```
    #10; sw=4'b1000;
```

## BEHAVIORAL SHEMA

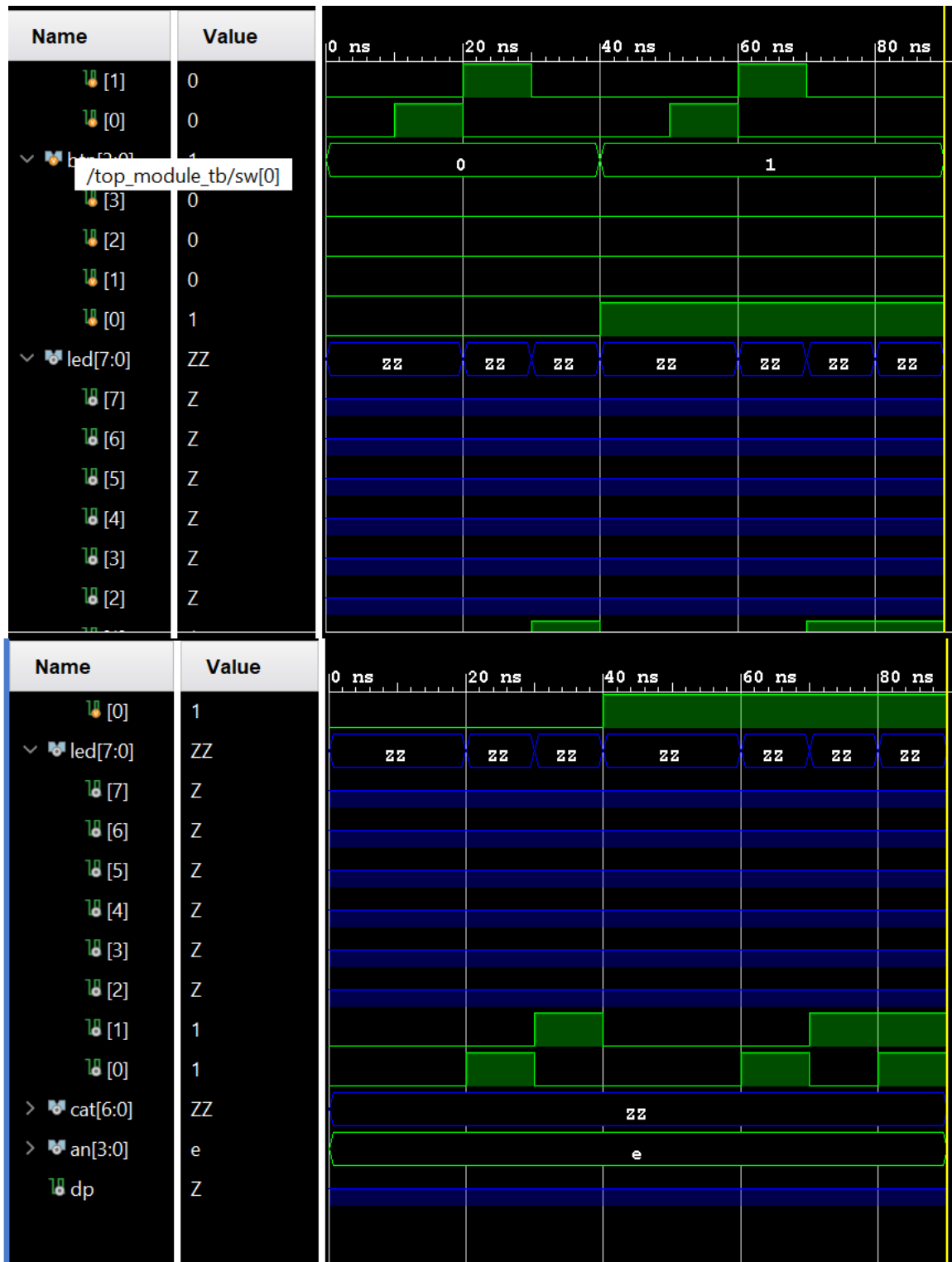

## RTL SHEMA

 

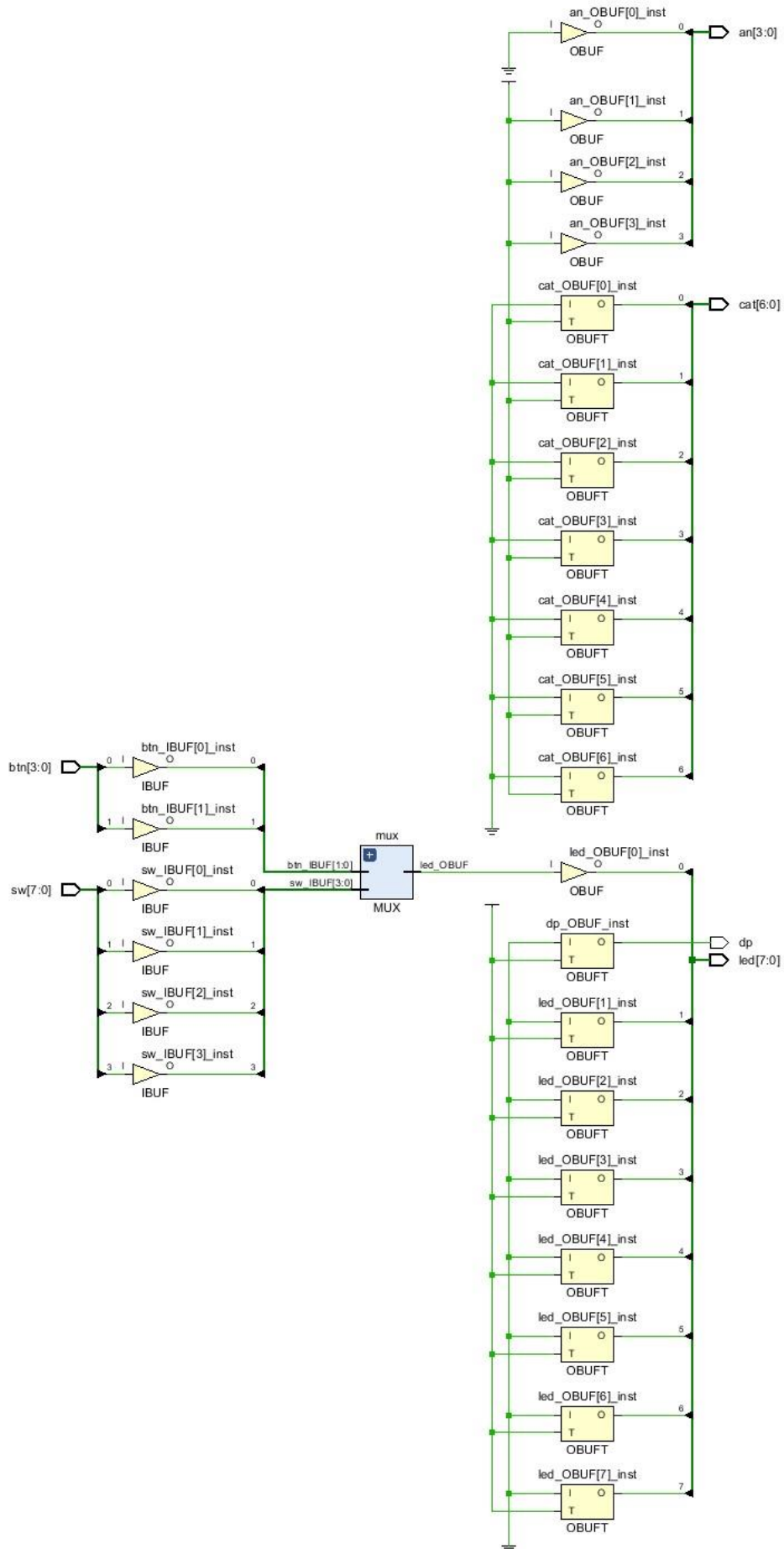


## TIMING COMPARE

From Port	To Port	Max Delay	Max Process Corner	Min Delay	Min Process Corner
btn[0]	led[0]	5.335	SLOW	2.073	FAST
btn[1]	led[0]	5.335	SLOW	2.073	FAST
sw[0]	led[0]	5.335	SLOW	2.073	FAST
sw[1]	led[0]	5.335	SLOW	2.073	FAST
sw[2]	led[0]	5.335	SLOW	2.073	FAST
sw[3]	led[0]	5.335	SLOW	2.073	FAST

From Port	To Port	Max Delay	Max Process Corner	Min Delay	Min Process Corner
btn[0]	led[0]	5.335	SLOW	2.073	FAST
btn[1]	led[0]	5.335	SLOW	2.073	FAST
sw[0]	led[0]	5.335	SLOW	2.073	FAST
sw[1]	led[0]	5.335	SLOW	2.073	FAST
sw[2]	led[0]	5.335	SLOW	2.073	FAST
sw[3]	led[0]	5.335	SLOW	2.073	FAST

## UTILIZATION COMPARE

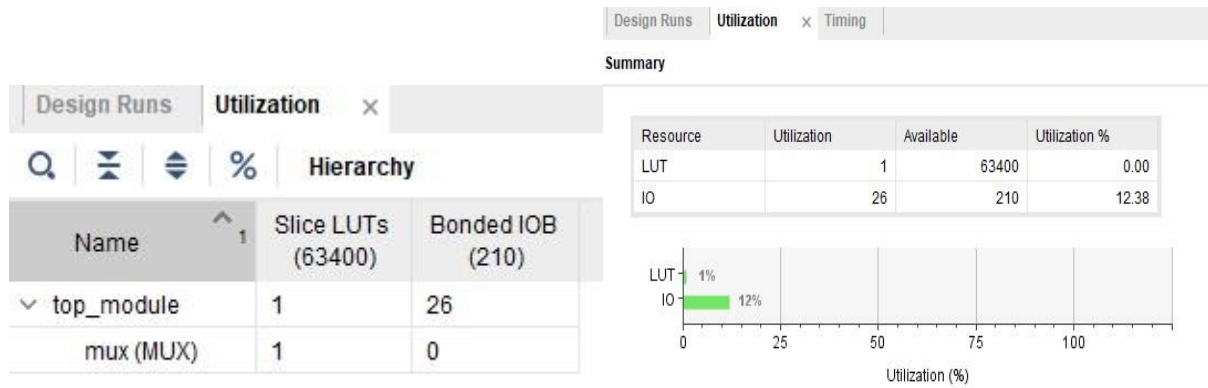

## DEMULTIPLEXER

### MSI LIBRARY

```

module DEMUX(
    input D,
    input S0,S1,
    output [3:0]O;
    wire [3:0]a;
    wire [3:0]b;

    NOT not2(.I1(S0),.O(a[0]));
    NOT not3(.I1(S1),.O(a[1]));
    AND and1(.I1(a[0]),.I2(a[1]),.O(b[0]));
    TRI tri2(.E(b[0]),.I(D),.O(O[0]));

    NOT not4(.I1(S1),.O(a[2]));
    AND and3(.I1(a[2]),.I2(S0),.O(b[1]));
    TRI tri3(.E(b[1]),.I(D),.O(O[1]));

    NOT not6(.I1(S0),.O(a[3]));
    AND and4(.I1(a[3]),.I2(S1),.O(b[2]));
    TRI tri4(.E(b[2]),.I(D),.O(O[2]));

```

### TOP MODULE

```

`timescale 1ns / 1ps
module top_module(
    input [7:0] sw,
    input [3:0] btn,
    output [7:0] led,
    output [6:0] cat,
    output [3:0] an,
    output dp
);
    assign an = 4'b1110;
    wire [15:0] new;
    assign dp = new[15];
    assign cat = new[14:8];
    assign led = new[7:0];

    //DECODER decoder1(.IN(sw[3:0]),.O(new));

```

## - TESTBENCH

```
`timescale 1ns / 1ps
module top_module_tb(
);
    reg [7:0] sw;
    reg [3:0] btn;
    wire [7:0] led;
    wire [6:0] cat;
    wire [3:0] an;
    wire dp;

    top_module uut(sw,btn,led,cat,an,dp);


    initial
    begin
        $finish;
    end

    //demux
    sw=1'b0; btn=2'd0;
    #10; sw=1'b0; btn=2'd1;
    #10; sw=1'b0; btn=2'd2;
    #10; sw=1'b0; btn=2'd3;

    sw=1'b1; btn=2'd0;
    #10; sw=1'b1; btn=2'd1;
```



## BEHAVIORAL SHEMA

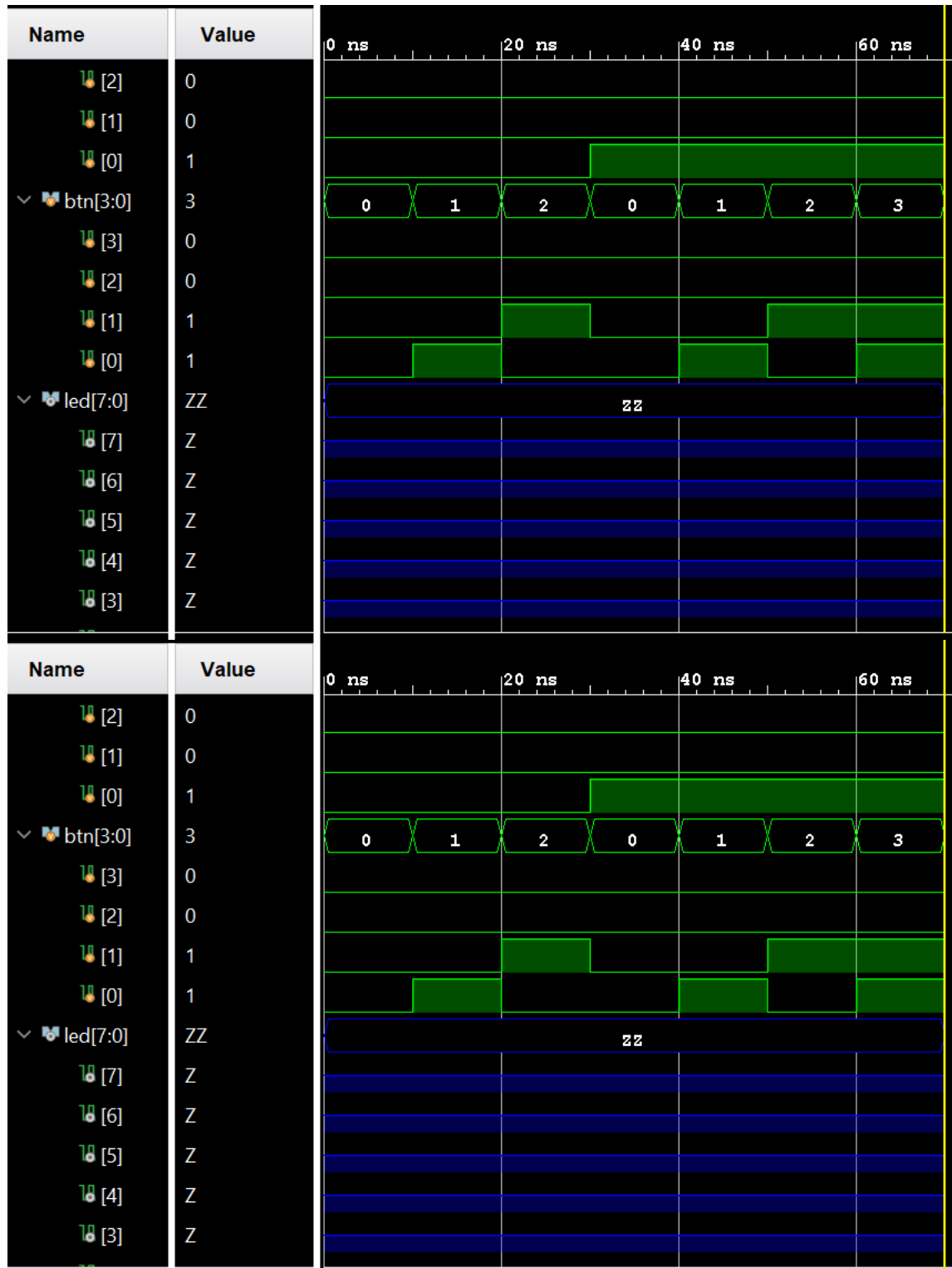

## RTL SHEMA

